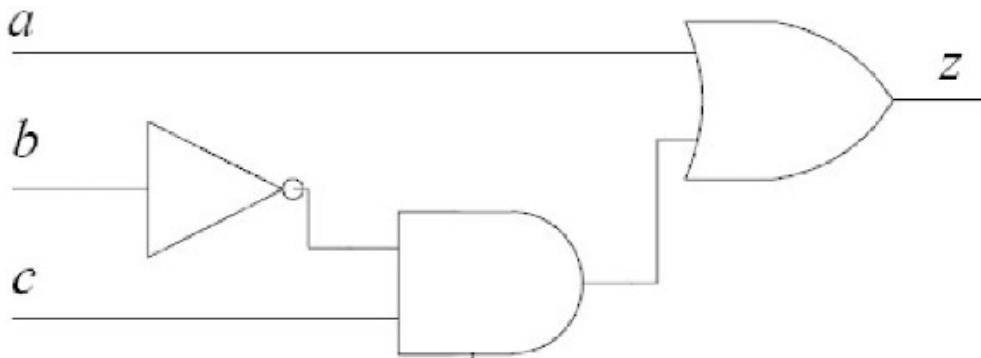


GATE

Prof.G V V Sharma

January 8, 2024

1. Consider the boolean Function $z(a, b, c)$.



(Gate CS-2020,28)

Which of the following minterm lists represent the circuit given above?

- (a) $z = \Sigma(0, 1, 3, 7)$
- (b) $z = \Sigma(1, 4, 5, 6, 7)$
- (c) $z = \Sigma(2, 4, 5, 6, 7)$
- (d) $z = \Sigma(2, 3, 5)$